

project2

- HalfAdder
- FullAdder
- Add16
- Inc16
- ALU

HalfAdder

真值表：

Half Adder			
a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

可以看出sum 是Xor(a,b)

而carry是 And(a, b)

```
1 // This file is part of www.nand2tetris.org
2 // and the book "The Elements of Computing Systems"
3 // by Nisan and Schocken, MIT Press.
4 // File name: projects/02/HalfAdder.hdl
5 /**
6  * Computes the sum of two bits.
7  */
10 CHIP HalfAdder {
11     IN a, b;    // 1-bit inputs
```

```


12     OUT sum,    // Right bit of a + b
13     carry;    // Left bit of a + b
14
15 PARTS:
16 // Put you code here:
17 And (a=a , b=b, out=carry );
18 Xor (a=a, b=b, out =sum);
19 }

```

21

FullAdder

真值表：

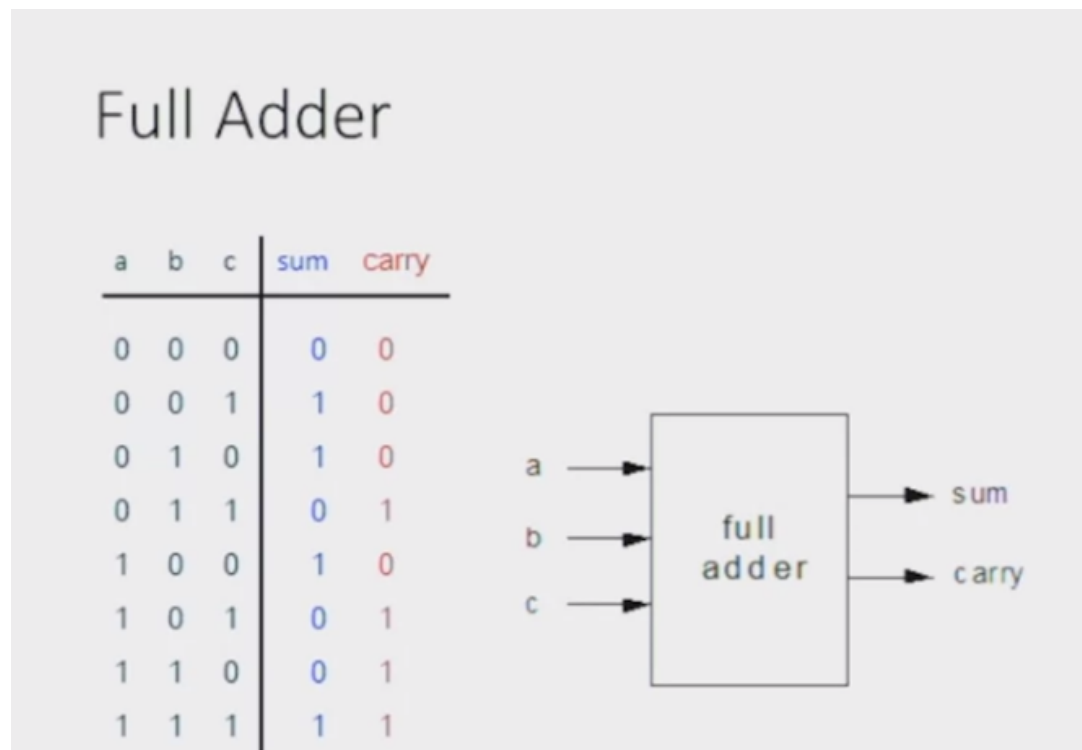

全加器就是有了一个进位a 即 $a+b+c$

可以考虑先将其HalfAdder(b,c)后, 得到sum1 和compare1

再HalfAdder(a,sum1) 得到sum, compare2

再HalfAdder(compare1,compare2)得到sum = compare

```

1 // This file is part of www.nand2tetris.org
2 // and the book "The Elements of Computing Systems"
3 // by Nisan and Schocken, MIT Press.
4 // File name: projects/02/FullAdder.hdl
5 /**
6  * Computes the sum of three bits.
7  */
8
9 CHIP FullAdder {
10     IN a, b, c; // 1-bit inputs
11     OUT sum,    // Right bit of a + b + c
12     carry;    // Left bit of a + b + c
13
14     PARTS:
15     // Put you code here:
16     HalfAdder( a = b ,b = c,sum = sum1 ,carry = carry1);
17     HalfAdder( a =a ,b = sum1,sum = sum ,carry = carry2);
18     HalfAdder( a =carry1 ,b = carry2,sum =carry ,carry = nothing);
19

```

Add16

16-bit Adder

out = a + b, as 16-bit integers
(overflow ignored)



```

1 // This file is part of www.nand2tetris.org
2 // and the book "The Elements of Computing Systems"
3 // by Nisan and Schocken, MIT Press.
4 // File name: projects/02/Adder16.hdl
5
6 /**
7  * Adds two 16-bit values.
8  * The most significant carry bit is ignored.
9  */
10 CHIP Add16 {
11     IN a[16], b[16];
12     OUT out[16];
13     PARTS:
14         // Put you code here:
15         HalfAdder(a = a[0], b = b[0], sum = out[0], carry = carry1);
16         FullAdder(a = carry1, b = a[1], c = b[1], sum = out[1], carry = carry2);
17         FullAdder(a = carry2, b = a[2], c = b[2], sum = out[2], carry = carry3);
18         FullAdder(a = carry3, b = a[3], c = b[3], sum = out[3], carry = carry4);
19         FullAdder(a = carry4, b = a[4], c = b[4], sum = out[4], carry = carry5);
20         FullAdder(a = carry5, b = a[5], c = b[5], sum = out[5], carry = carry6);
21         FullAdder(a = carry6, b = a[6], c = b[6], sum = out[6], carry = carry7);
22         FullAdder(a = carry7, b = a[7], c = b[7], sum = out[7], carry = carry8);
23         FullAdder(a = carry8, b = a[8], c = b[8], sum = out[8], carry = carry9);
24         FullAdder(a = carry9, b = a[9], c = b[9], sum = out[9], carry = carry10);
25         FullAdder(a = carry10, b = a[10], c = b[10], sum = out[10], carry = carry11);
26         FullAdder(a = carry11, b = a[11], c = b[11], sum = out[11], carry = carry12);
27         FullAdder(a = carry12, b = a[12], c = b[12], sum = out[12], carry = carry13);
28         FullAdder(a = carry13, b = a[13], c = b[13], sum = out[13], carry = carry14);
29         FullAdder(a = carry14, b = a[14], c = b[14], sum = out[14], carry = carry15);
30

```

```

32 FullAdder(a = carry15 ,b= a[15],c =b[15],sum=out[15],carry =nothing);
33 }

```

Inc16

就是加一，只需要注意语法上的实现

```

1 // This file is part of www.nand2tetris.org
2 // and the book "The Elements of Computing Systems"
3 // by Nisan and Schocken, MIT Press.
4 // File name: projects/02/Inc16.hdl
5 /**
6  * 16-bit incrementer:
7  * out = in + 1 (arithmetic addition)
8  */
9
10 CHIP Inc16 {
11     IN in[16];
12     OUT out[16];
13     PARTS:
14     // Put your code here:
15     Add16(a = in,b[0] = true,b[1..15]=false,out=out);
16 }

```

ALU

我遇到的问题是内部的接口似乎无法切片（[0..3]这种操作）？

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

```

1 // This file is part of www.nand2tetris.org

```

```

2 // and the book "The Elements of Computing Systems"
3 // by Nisan and Schocken, MIT Press.
4 // File name: projects/02/ALU.hdl
5
6 /**
7  * The ALU (Arithmetic Logic Unit).
8  * Computes one of the following functions:
9  * x+y, x-y, y-x, 0, 1, -1, x, y, -x, -y, !x, !y,
10 * x+1, y+1, x-1, y-1, x&y, x|y on two 16-bit inputs,
11 * according to 6 input bits denoted zx,nx,zy,ny,f,no.
12 * In addition, the ALU computes two 1-bit outputs:
13 * if the ALU output == 0, zr is set to 1; otherwise zr is set to 0;
14 * if the ALU output < 0, ng is set to 1; otherwise ng is set to 0.
15 */
16 // Implementation: the ALU logic manipulates the x and y inputs
17 // and operates on the resulting values, as follows:
18 // if (zx == 1) set x = 0 // 16-bit constant
19 // if (nx == 1) set x = !x // bitwise not
20 // if (zy == 1) set y = 0 // 16-bit constant
21 // if (ny == 1) set y = !y // bitwise not
22 // if (f == 1) set out = x + y // integer 2's complement addition
23 // if (f == 0) set out = x & y // bitwise and
24 // if (no == 1) set out = !out // bitwise not
25 // if (out == 0) set zr = 1
26 // if (out < 0) set ng = 1
27
28 CHIP ALU {
29     IN
30         x[16], y[16], // 16-bit inputs
31         zx, // zero the x input?
32         nx, // negate the x input?
33         zy, // zero the y input?
34         ny, // negate the y input?
35         f, // compute out = x + y (if 1) or x & y (if 0)
36         no; // negate the out output?
37
38     OUT
39         out[16], // 16-bit output
40         zr, // 1 if (out == 0), 0 otherwise
41         ng; // 1 if (out < 0), 0 otherwise
42
43     PARTS:
44         // Put your code here:
45         //process zx nx
46         Mux16(a=x ,b= false,sel = zx,out = xval);
47         Not16(in=xval, out=notx);
48         Mux16(a=xval ,b= notx,sel = nx,out = lastx);
49         //process zy ny
50         Mux16(a=y ,b= false,sel = zy,out = yval);
51         Not16(in = yval,out = noty);
52         Mux16(a=yval ,b= noty,sel = ny,out = lasty);
53         //pocsee f
54         And16(a=lastx,b=lasty,out = Andf);

```

```
59     Add16(a=lastx,b=lasty,out = Addf);
60     Mux16(a =Andf,b = Addf,sel=f,out = outMux);
61
62     //process no
63     Not16(in = outMux,out = outNot);
64     Mux16(a =outMux,b=outNot,sel = no,out =out1);
65
66     //set zr
67     Or16Way(in=out1,out=orlast);
68     Mux(a=true,b=false,sel=orlast,out =zr);
69
70     //set ng
71     IsNeg(in=out1,out =ng);
72     Or16(a=out1,b=false,out=out);
73
74
75 }
```